
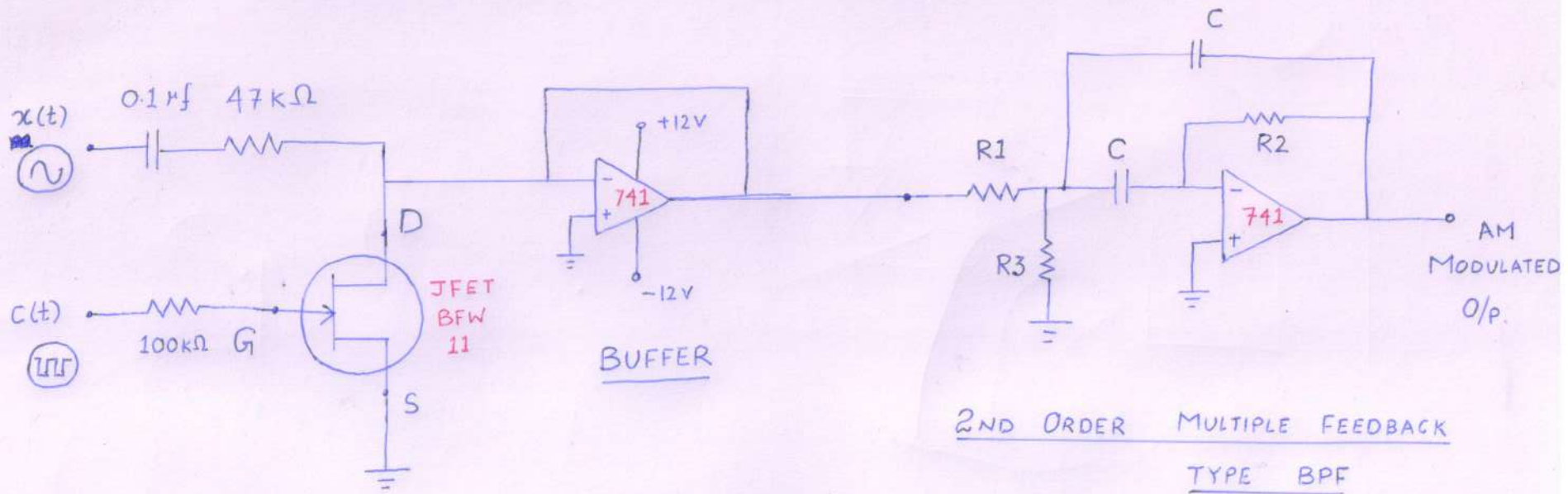


SWITCHING MODULATOR USING A TRANSISTOR

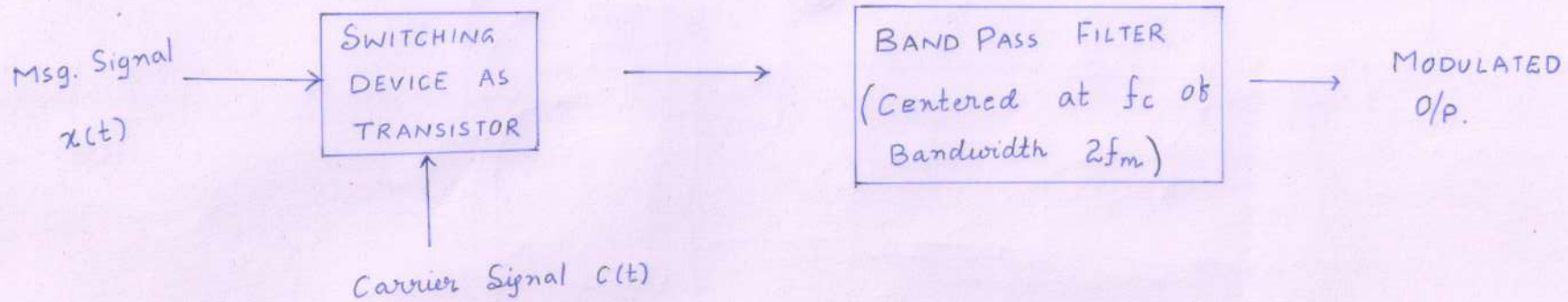

$x(t)$ = Sine Signal, $4V_{pp}$, $f_m = 1\text{ KHz}$

$c(t)$ = Pulse Signal (Duty Cycle = 50%)

